

# Computer Aided Digital System Design (99-00-1)

Dr. Hajar Falahati

Homework 4: Technology Mapping, Synthesis			
<b>Deadline:</b> 1399/11/02 23:59			
Problem	Definition	Credit	Your Mark
P1	SPLD	30	
P2	FPGA Synthesis	40	
P3	<b>Synthesis Rules</b>	30	
Total		100	

# **Required File:**

Upload a zip file titled as "CAD-HW4- Student numberi- ...- Student numberj".

## **Contact Information:**

Ask your questions via the course website or send an email to:

hosseinaminiii75@gmail.com hosseini99.zahra@gmail.com hfalahati@ipm.ir


#### 1- SPLD: Simple Programmable Logic Device [30 points]

Design a circuit which gets a non-negative 4-bit input and return 1 when the input is divisible by 3.


- i. Implement the circuit by a ROM with 4 input lines and two output lines. [10 points]
- ii. Implement the circuit by a PLA consisting of 4 input lines and two output lines. [10 points]
- iii. Implement the circuit by a PAL consisting of 4 input lines, four 2-input OR. The OR output and its complement are sent back to the logic. [10 points]

#### 2- FPGA Synthesis [40 points]

 - i. Implement a protein detector which detect the LDLD protein using the FPGA whose basic block is shown in the following.
  - Hint 1: Draw the FSM at first.
  - Hint 2: You have already drawn the FSM!



 ii. Implement the function  $f = B + (A + \bar{C}) \cdot (\bar{A} + \bar{B} + \bar{C})$  on the following mux-based FPGA.



## 3- Synthesis Rules [30 points]

Suppose you have all the logic resources. Synthesis the following codes and elaborate if there are any mistakes. Determine the type of errors

i. Code 1: (For example, i++ is wrong, replace it by i=i+1. Suppose 1 < n < 4)

```
always @ (A or B)
begin
for (i = 0; i < n; i++)
begin
M[i] = A[i] * B[i];
PS[i] = PS[i] + M[i];
end
```

#### ii. Code 2

```
Module concatination2 (input clk, input dataIn1, input dataIn2, output [1:0] dataO);

always @ (posedge clk, data_in1)
        if (data_in1)
            dataO = {dataIn1, dataIn2};
        else if (data_in2)
            dataO = {dataIn2, dataIn1};

endmodule
```