

# Computer-Aided Design

99-00-1

Dr. Falahati



Final

1399/11/04


150 minutes

Problem	Definition	Credit	Your Mark
P1	Verilog Coding & Synthesis	50	
P2	Code Analysis	25	
P3	SPLD	15	
P4	Modular Coding	20	
Total		110	

1. The exam time is 150 minutes.
2. Check the exam problems and ask your questions during the first 5 minutes.
3. Do not ask any question after 5 minutes!
4. The exam is open book!
5. Write the final answer clearly.
6. Write all your work. It helps you to get some portions of credits.
7. Good Luck
 
## P1. Verilog Coding and Synthesis [50 points]

Consider a sequential frequency divider which generates three signals with different frequencies. The frequencies of  $f1$ ,  $f2$ , and  $f3$  are 1,  $\frac{1}{2}$ , and  $\frac{1}{4}$  of  $CLK$  frequency, respectively.




**Q1.** [20 points] Write a behavior-level Verilog. Your implementation instances two modules:

- “calculate-next-state”: a gate-level module to calculate the next state.
- “calculate-output”: a dataflow-level module to calculate the outputs  $f1$ ,  $f2$ , and  $f3$ .

**Q2.** [10 points] Write a test module and check the validity of your code.

**Q3.** [10 points] Synthesis the frequency divider module using the logic gates and FFs. Suppose you have any kinds of logic gates and J-K FFs.

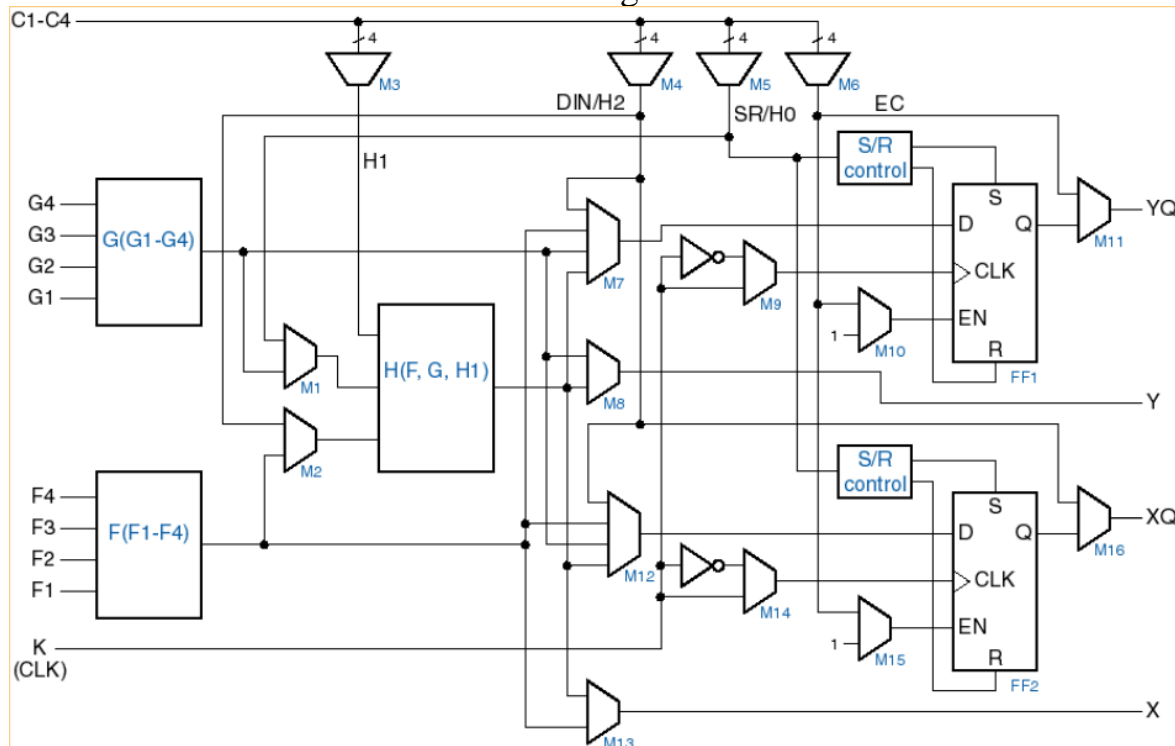**Q4.** [10 points] Synthesis the frequency divider module using the FPGA whose basic block is shown in the following.



## P2. Code Analysis [25 Points]

Consider the following codes and answer the questions:

**Q1.** [5 points] Does the following code implement a combinational or sequential circuit? Support your response

```

Module sample1 (input clk, input dataIn1, input dataIn2, output reg [1:0] dataO);
    always @ (posedge clk, data_in1)
        if (data_in1)
            dataO = {dataIn1, dataIn2};
        else if (data_in2)
            dataO = {dataIn2, dataIn1};

endmodule

```

**Q2.** [10 points] Suppose you have all the logical gates and FFs, synthesis the sample 1.

**Q3.** [10 points] What is the output of the following code after one CLK cycle and the initial value of a = 8'hE3, b = 4'd1, and c = 4'o 3

```

Module sample2 (input clk, input [3:0] b, input [3:0] c, output reg [7:0] a);
    always @ (negedge clk)
        begin
            a <= {a, &b, |c};
            a[0] <= ^a [7:6];
        end
endmodule

```

### **P3. Simple Programmable Logic Device [15 points]**

**Q1.** [5 points] Draw a PAL-based SPLD to implement 3-input functions (i.e.,  $f(x_1, x_2, x_3)$ ). The PAL consists of two 2-input OR. The OR outputs and their complements are sent back to the PAL.

**Q2.** [10 points] Implement these two functions on the PAL with minimum number of resources.

$$f_1(x_1, x_2, x_3) = x_1 \overline{x_2} \overline{x_3} + \overline{x_1} x_2 \overline{x_3} + x_1 x_2 \overline{x_3} + x_3 x_1 + x_3 x_2$$

$$f_2(x_1, x_2, x_3) = x_1 \overline{x_3} + x_2 \overline{x_3} + \overline{x_1} \overline{x_2} x_3$$

### **P4. Modular Coding [20 points]**

Complete the following module to calculate the Fibonacci number using function.

$$F(n) = F(n - 1) + F(n - 2) \quad F(1) = 1, \quad F(2) = 1$$

```

module Fibonacci (input [2:0] n, output [4:0] Fibo);

endmodule

```